

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III(OLD) • EXAMINATION – WINTER 2016

Subject Code:130902

Date:02/01/2017

Subject Name:Analog and Digital Electronics

Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List and Discuss all ideal characteristics of an Op Amp. **07**
(b) Explain block diagram of OP-AMP. Explain function of each block. **07**
- Q.2** (a) What is CMRR? What is effect of frequency on CMRR? **07**
(b) Enlist the applications of 555 timer in astable and monostable mode. **07**
- OR**
- (b) Explain integrator with its frequency response. **07**
- Q.3** (a) Draw functional block diagram of IC 555 & discuss function of each pin. **07**
(b) Realize EX-OR and NOR gate using NAND gate. **07**
- OR**
- Q.3** (a) Explain principle of Basic Comparator. Describe operation of Schmitt Trigger with necessary diagram. **07**
(b) Minimize the following Boolean expression using K-map and realize it using AOI gates. $Y = \sum m(0,1,5,9,13,14,15) + d(3,4,7,10,11)$ **07**
- Q.4** (a) Explain edge triggered D Flip flop with its truth table. Also state its applications. **07**
(b) Explain RTL and I²R logic families. **07**
- OR**
- Q.4** (a) Describe operation of D/A converter with binary-weighted resistors **07**
(b) Define encoders, decoders, multiplexer and de-multiplexer. Give application of each. **07**
- Q.5** (a) Design BCD to seven segment decoder for common anode display. **07**
(b) Write down modes of operation of shift register. Explain any one mode of operation in detail. **07**
- OR**
- Q.5** (a) What is PLL? Discuss different applications of PLL in detail. **07**
(b) Explain the use of op-amp as a zero crossing detector with neat sketch. **07**
