

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) - EXAMINATION – SUMMER 2018

Subject Code:2130902

Date:23/05/2018

Subject Name:Analog Electronics

Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Draw block-diagram representation of a typical op-amp.	03
	(b) Define: (1) PSRR (2) Input bias current (3) Input offset voltage (4) SVRR.	04
	(c) Draw the IC-555 based astable multivibrator circuit and derive equation for frequency of output waveform.	07
Q.2	(a) Draw transistor C-E amplifier circuit. Draw its ac equivalent circuit.	03
	(b) Draw and explain stages of instrumentation amplifier.	04
	(c) Explain how Op-amp works as an average amplifier.	07
	OR	
	(c) What is transistor load line? Explain how to obtain it. Define Q- point on the load line.	07
Q.3	(a) Draw and explain OP-AMP as a zero crossing detector.	03
	(b) Give comparison of: astable, monostable and bistable multivibrator.	04
	(c) What do you mean by slew rate in an OP-AMP? Also mention about causes of slew rate and explain its significance in applications.	07
	OR	
Q.3	(a) Compare various transistor amplifier configurations.	03
	(b) What is power amplifier? Give important features of power amplifier circuit.	04
	(c) What will be effect of voltage series feedback amplifier on input resistance, gain and stability?	07
Q.4	(a) What are the merits & demerits of hybrid parameters?	03
	(b) Compare different types of power transistors.	04
	(c) Classify the types of negative feedback & explain each in brief.	07
	OR	
Q.4	(a) What are the applications of OP- AMP based schmitt trigger circuit.	03
	(b) Explain application of OP-AMP based Wein bridge oscillator.	04
	(c) With the help of neat diagram explain the circuit of voltage to current converter. Also state its applications.	07
Q.5	(a) Compare between active and passive filters.	03
	(b) Explain with the help of circuit diagram, the operation of second order Butterworth high pass filter.	04
	(c) Discuss the operation of LM317 voltage regulator.	07

OR

- Q.5**
- (a)** List out the different performance parameter of a power supply. **03**
 - (b)** Draw basic block schematic of 78×× series three terminal voltage regulator ICs. **04**
 - (c)** What is PLL? Discuss different applications of PLL in detail. **07**
