

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) - EXAMINATION – SUMMER 2018

Subject Code:2131006

Date:23/05/2018

Subject Name:Electronic Devices and Circuits


Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Explain operation of class B-push pull amplifier with the help of circuit and wave form.	03
	(b) Explain p and n semiconductor formation in detail.	04
	(c) Explain Voltage Divider Bias biasing in detail.	07
Q.2	(a) What is bulk resistance? Find the bulk resistance of diode 1N4001 whose forward voltage and current is 0.93 V and 1 A respectively.	03
	(b) Differentiate FET and BJT.	04
	(c) Draw and explain series and shunt positive clipper with output waveforms.	07
	OR	
	(c) Give the advantages of Full wave bridge rectifier over center tap rectifier. Explain bridge rectifier with neat diagram. Also draw load voltage, load current, diode voltage waveforms.	07
Q.3	(a) Explain the function of LED with neat sketch.	03
	(b) Define following terms.	04
	1. Reverse saturation current	
	2. Surface leakage current	
	4. Peak inverse voltage	
	5. Surge current	
	(c) Give the importance of voltage multiplier. Explain voltage quadruple in detail.	07
	OR	
Q.3	(a) A zener regulator has an input voltage that may vary from 22 to 30 V. If the regulated output voltage is 12 V and the load resistance varies from 140 V to 10 kV, what is the maximum allowable series resistance	03
	(b) Draw V-I characteristics of Zener diode.	04
	(c) What value should R2 be in figure below to set up a diode current of 0.25 mA? Consider $V_D=0.7V$	07

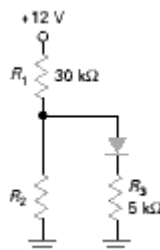

- Q.4** (a) Explain transistor construction with size and doping level of each region. **03**
(b) Explain transistor characteristics with clearly indicating saturation, active and cut off region. **04**
(c) Explain Darlington pair in detail. Also derive its current gain. **07**

OR

- Q.4** (a) Derive relation between α_{dc} and β_{dc} of a transistor **03**
(b) Draw and explain the input and output characteristics of common emitter configuration. **04**
(c) Explain the working of emitter follower. Draw the ac equivalent circuit and determine the AC emitter resistance, voltage gain and input impedance. **07**
- Q.5** (a) Compare E MOSFET with D MOSFET. **03**
(b) Explain JFET as an amplifier. **04**
(c) Define positive and negative feedback. Also derive the expression of transfer gain with negative feedback with the use of block diagram. **07**

OR

- Q.5** (a) Compare the power amplifier by its operation cycle. **03**
(b) Define four type of negative feedback amplifier. **04**
(c) Explain the construction and operation of n type JFET. **07**
