

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III(New) • EXAMINATION – WINTER 2016

Subject Code:2131006

Date:04/01/2017

Subject Name:Electronic Devices and Circuits

Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1 Short Questions

14

- 1 Knee voltage of germanium diode is _____ then silicon diode.
- 2 In reverse bias current through diode is very _____.
- 3 Frequency of full wave rectified voltage is _____.
- 4 If filter capacitance increased, diode forward bias period _____.
- 5 Varactor diode is used in _____ bias.
- 6 Size of collector is _____ compare to emitter.
- 7 Transistor is on when it is operating in _____ region.
- 8 Transistor collector current is _____ when it is operating in cut off region.
- 9 For emitter bias, voltage at emitter is 0.7 less then _____ voltage.
- 10 Current in a coupling capacitor circuit for high frequencies is _____.
- 11 Input impedance of the base of an emitter follower is _____.
- 12 Audio amplifier operates in frequency range of _____.
- 13 A JFET is _____ controlled device.
- 14 Full form of CMOS is _____.

- Q.2**
- (a) Draw and explain full wave bridge rectifier. **04**
 - (b) Due to any cause R becomes 0 in fig. 1. What will be effect on diode and what will be diode voltage? **03**
 - (c) In fig. 2 what is maximum positive and negative output voltage? Sketch the output waveforms. **07**

OR

- (c) Draw half wave rectifier circuit. Draw waveform for voltage across diode, diode current with R and RC load. **07**
- Q.3**
- (a) Explain transistor construction with size and doping level of each region. **03**
 - (b) What is voltage divider bias? What is its disadvantage? How it is removed with emitter bias? **07**
 - (c) What is base, collector and emitter voltage in fig.3. **04**

OR

- Q.3**
- (a) How transistor act as a switch? What are limitations? **03**
 - (b) What is I_{CQ} , V_{CEQ} and r_c in fig. 4. **04**
 - (c) Explain transistor characteristics with clearly indicating saturation, active and cut off region. How load line is drawn in characteristics. **07**
- Q.4**
- (a) Explain Class AB operation of power amplifier. **03**
 - (b) Explain small signal common emitter amplifier. **04**
 - (c) Transistor in fig.5 has current gain of 150 and zener voltage 7.5.What is output voltage, zener current and transistor power dissipation. **07**

OR

- Q.4**
- (a) Explain Class A operation of power amplifier. **03**
 - (b) Explain small signal common collector amplifier. **04**
 - (c) Draw ac equivalent circuit of fig. 6. **07**

- Q.5**
- (a) Explain thermal runaway with respect to MOSFET. **03**

- (b) What is negative and positive feedback?

04
- (c) Explain construction, operation and characteristics of JFET.

07

OR

- Q.5 (a) What are advantages of JFET over Bipolar Junction Transistor?

03
- (b) How JFET are biased?

04
- (c) What are different four types of feedback?

07

