

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VI (NEW) - EXAMINATION – SUMMER 2016

Subject Code:2160902

Date:11/05/2016

Subject Name: Power Electronics – II

Time: 10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Explain 3 phase inverter operation for 180° with the gate voltage and phase voltage waveform. **07**
- (b)** What are line commutated inverters? How do they operate? Explain the difference between line commutated and force commutated inverters. **07**
- Q.2 (a)** List various PWM methods used in inverters for Harmonic reduction and explain Sinusoidal Pulse Modulation with necessary waveforms. **07**
- (b)** Describe the working of a single phase half bridge inverter. What is its main drawback? Explain how this drawback is overcome. **07**
- OR**
- (b)** Describe the working of a single phase parallel inverter with relevant circuit and waveforms. **07**
- Q.3 (a)** Explain the working of single phase ac voltage controller catering R-L load, along with the needed waveform. Derive its equation for the average output voltages. **07**
- (b)** Describe the working of a two stage sequence control of voltage controller for both R and RL load. **07**
- OR**
- Q.3 (a)** What is an AC voltage controller? A single phase voltage controller using two SCRs in antiparallel must have its trigger sources isolated from each other. Why? Explain with suitable diagram. **07**
- (b)** A single phase voltage controller has input voltage of 230V, 50Hz and a load of $R=15\Omega$. For 6 cycle on and 4 cycle off, determine (a) rms output voltage, (b) input power factor, (c) average and rms thyristor currents. **07**
- Q.4 (a)** Explain the basic principle of operation of a cycloconverter with neat equivalent circuit diagram. **07**
- (b)** What is load commutated cycloconverter? How does it differ from line commutated cycloconverter? **07**
- OR**
- Q.4 (a)** Give the comparison between a cycloconverter and a dc link converter. **07**
- (b)** A three pulse cycloconverter feeds a single phase load of 190V, 45A at a power factor of 0.7 lagging. Determine: (a) the required supply voltage, (b) thyristor RMS current and PIV (c) power factor of the supply current. **07**
- Q.5 (a)** Write a short note on V/F control of an induction motor.. **07**
- (b)** Draw the neat circuit diagram and explain the speed control of 3 phase induction motor by rotor resistance control method using chopper. **07**
- OR**
- Q.5 (a)** Write a note on speed control of Synchronous motor employing cycloconverter. **07**

(b) Explain the close loop control of induction motor.

07
