

GUJARAT TECHNOLOGICAL UNIVERSITY
BE – SEMESTER – VI (NEW).EXAMINATION – WINTER 2016

Subject Code: 2160902

Date: 25/10/2016

Subject Name: Power Electronics – II

Time: 10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State the merits & demerits of current source inverter & voltage source inverter. **07**
(b) What are the methods of speed control of induction motor? Explain any one method in detail. **07**
- Q.2** (a) Explain 1- ϕ full-wave AC controller with circuit diagram and wave form. **07**
(b) Distinguish series inverter and parallel inverter. **07**
- OR**
- (b) Explain Sine wave PWM technique. What is the effect of modulation index on output? Explain its merit and demerit. **07**
- Q.3** (a) Explain the working principle of 1- ϕ cycloconverter. **07**
(b) Explain 120 degree mode of 3- ϕ bridge inverter with resistive load. **07**
- OR**
- Q.3** (a) Explain 180 degree mode of operation for 3- ϕ bridge inverter with resistive load. **07**
(b) Explain 3- ϕ Cycloconverter. **07**
- Q.4** (a) Explain full bridge topology of 1- ϕ bridge inverter with resistive load. **07**
(b) Explain 3- ϕ Synchronous Motor Drives using variable frequency control technique. **07**
- OR**
- Q.4** (a) Explain rotor resistive control for induction motor using power electronics device. **07**
(b) Explain constant V/F control with the help of block diagram for Induction motor. **07**
- Q.5** (a) Explain Stator voltage control with AC voltage controller for 3- ϕ Induction Motor drive. **07**
(b) Give classification of different techniques for voltage control of inverter. Explain any one. **07**
- OR**
- Q.5** (a) Explain working of Matrix AC to AC converter. **07**
(b) Comparison of ac & dc drive and their selection for particular application. **07**
