GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII (OLD) EXAMINATION - SUMMER 2019

Subject Code: 170906 Date: 10/05/2019

Subject Name: Advanced Power Electronics - I

Time: 02:30 PM TO 05:00 PM **Total Marks: 70**

Instructions:

- 1. Attempt all questions.
- Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- **Q.1 07** (a) Explain basic series load resonance converter with necessary circuit diagram and waveforms.
 - (b) Explain operation of 12-pulse converter with circuit diagram and necessary **07** waveforms.
- (a) Discuss basic concept of multilevel inverter. Write advantages and disadvantages 07 **Q.2** of multilevel inverter.
 - (b) List the separate DC sources used for cascaded multilevel inverter. Explain **07** operation of five level cascaded multilevel inverter.

- (b) Discuss operation of three level diode clampled multilevel inverter **07**
- Explain Y-Z1 transformer connection used for multipulse converter. **Q.3** 07
 - (b) List application of multipulse converter. Draw the transformer connections for 07 18 and 24 pulse converter.

OR

- Discuss operation of flying capacitor multilevel inverter. **07** 0.3 (a)
 - **(b)** Compare multipulse converter with multilevel inverter.
- Explain working of forward converter based switch mode power supply. 07 **Q.4** (a) 07
- Discuss two quadrant ZVS converter with necessary circuit diagram and waveforms.

OR

- Discuss push pull converter and its application in dc power supply. 0.4 (a) 07 07
 - Explain operation of ZCS converter with diagram and wave forms.
- Explain operation and control of On-Line and Off-Line UPS. 07 Q.5 (a)
 - Discuss working and operation of Brushless dc motor. Show derivation of switching pulses using Hall sensor signals.

- Discuss phenomenon of electromechanical energy conversion in SRM. Q.5
 - (b) With neat circuit diagram and waveform discuss class E resonant inverter.

07

07

07

07