

GUJARAT TECHNOLOGICAL UNIVERSITY
BE – SEMESTER VII-(NEW SYLLABUS) EXAMINATION- SUMMER - 2018

Subject Code: 2170906

Date: 28/04/2018

Subject Name: Advanced Power Electronics (Departmental Elective - II)

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Explain operation of boost converter with neat circuit diagram.	03
	(b) Define FACTS. Give classification of FACTS controllers.	04
	(c) Describe Cuk converter with circuit diagram.	07
Q.2	(a) Explain fly back converter topology with diagram and wave forms.	03
	(b) Compare ZVS-ZCS converter.	04
	(c) Explain principle of shunt compensation used for transmission line.	07
	OR	
	(c) Explain working of Diode Clamped three level inverter.	07
Q.3	(a) Classify resonant pulse converter and discuss applications.	03
	(b) Explain operation of Cascaded H-bridge multilevel inverter.	04
	(c) Draw circuit diagram and output voltage phasor diagram of 12-pulse converter.	07
	OR	
Q.3	(a) State advantages and disadvantages of multi-pulse converters.	03
	(b) Discuss Equipment required for HVDC System and their significance.	04
	(c) Discuss importance of reactive power compensation. Discuss phase-shifting transformer with necessary diagram in brief.	07
Q.4	(a) Comparison of EHVAC and HVDC transmission system.	03
	(b) Classify carrier based PWM technique for multilevel inverter. Discuss any one in detail.	04
	(c) Explain five level flying capacitor type multi-level inverter. What are demerits of this topology?	07
	OR	
Q.4	(a) Explain the working of Fixed Capacitor Thyristor-Controlled Reactor (FC-TCR). Draw neat diagrams.	03
	(b) Describe SEPIC converter with circuit diagram.	04
	(c) Explain working of STATCOM with neat diagram.	07
Q.5	(a) What is series compensation. Discuss working of Thyristor-controlled series capacitor (TCSC).	03
	(b) What is phase angle compensation in transmission system?	04
	(c) Explain working of Static Synchronous Series Compensator (SSSC) with neat diagrams.	07
	OR	
Q.5	(a) Explain working of forward converter with diagram and wave forms.	03
	(b) With neat circuit diagram and waveform discuss class E resonant inverter.	04
	(c) Explain operating principle of Unified power flow controller (UPFC).	07
